 


Title: Simulate a Full Adder in VHDL.

Problem Description: Develop a program in Verilog to perform full adder operation.

Full adder

```
module Fulladder12(sum,cout,a,b,c);  
input a,b,c;  
output sum,cout;  
assign sum=a^b^c;  
assign cout=(a&b)|(b&c)|(c&a);  
endmodule;
```



Title: Simulate a 8:1 MUX in VHDL

Problem Description: Develop a program in VHDL to perform 8:1 multiplexer operation.

```
module m81(out, D0, D1, D2, D3, D4, D5, D6, D7, S0, S1, S2);  
input wire D0, D1, D2, D3, D4, D5, D6, D7, S0, S1, S2;  
output reg out;  
always@(*)  
begin  
case({S0,S1,S2})  
3'b000: out=D0;
```

```

3'b001: out=D1;

3'b010: out=D2;

3'b011: out=D3;

3'b100: out=D4;

3'b101: out=D5;

3'b110: out=D6;

3'b111: out=D7;


default: out=1'b0;

endcase

end

endmodule

```

 

Title: Simulate a Flip-Flops in VHDL.

Problem Description: Develop a program in VHDL to check the working of flip-flops (JK/D/T)

```

module jk_ff ( input j, input k, input clk, output reg q);

    initial begin

q=0;

end

```

```
always @ (posedge clk)
```

```
begin
```

```
    case ({j,k})
```

```
        2'b00 : q <= q;
```

```
        2'b01 : q <= 0;
```

```
        2'b10 : q <= 1;
```

```
        2'b11 : q <= ~q;
```

```
    endcase
```

```
end
```

```
endmodule
```



Counter

Title: Simulate a 4-bit binary counter VHDL program.

Problem Description: Develop a program in VHDL to check 4-bit binary counter.

```

module counter (input clk,    // Declare input port for the clock to allow counter to count up
                input rstn,    // Declare input port for the reset to allow the counter to be reset to 0
                                when required
                output reg[3:0] out); // Declare 4-bit output port to get the counter values

// This always block will be triggered at the rising edge of clk (0->1)
// Once inside this block, it checks if the reset is 0, then change out to zero
// If reset is 1, then the design should be allowed to count up, so increment the counter

always @ (posedge clk) begin
    if (! rstn)
        out <= 0;
    else
        out <= out + 1;
end
endmodule

```



Ripple carry adder

Title: Simulate a 4-bit binary counter VHDL program.

Problem Description: Develop a program in VHDL to check 4-bit binary counter.

```

module rippe_adder(X, Y, S, Co);

```

```

input [3:0] X, Y;// Two 4-bit inputs

output [3:0] S;

output Co;

wire w1, w2, w3;

// instantiating 4 1-bit full adders in Verilog

fulladder u1(X[0], Y[0], 1'b0, S[0], w1);

fulladder u2(X[1], Y[1], w1, S[1], w2);

fulladder u3(X[2], Y[2], w2, S[2], w3);

fulladder u4(X[3], Y[3], w3, S[3], Co);


endmodule

```

```

module Fulladder12(a,b,c,sum,cout,);
input a,b,c;
output sum,cout;
assign sum=a^b^c;
assign cout=(a&b)|(b&c)|(c&a);
endmodule;

```

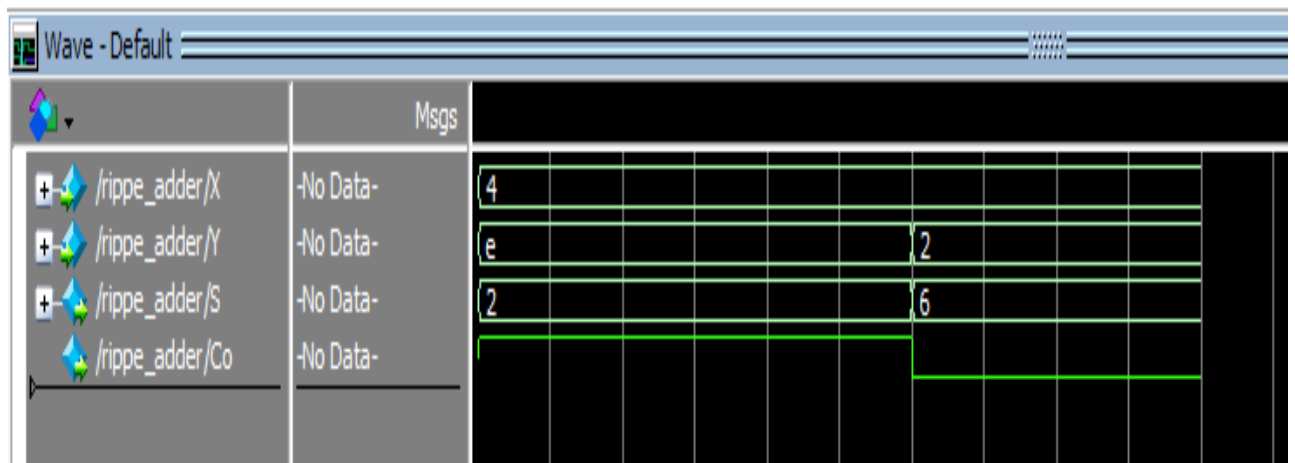

4 bit ALU

Title: Design of a 4-bit ALU.

Problem Description: Develop a program in VHDL to perform 4-bit ALU.

```

module alu(
    input [7:0] A,B, // ALU 8-bit Inputs
    input [3:0] ALU_Sel, // ALU Selection
    output [7:0] ALU_Out, // ALU 8-bit Output
    output CarryOut // Carry Out Flag
);
reg [7:0] ALU_Result;
wire [8:0] tmp;
assign ALU_Out = ALU_Result; // ALU out
assign tmp = {1'b0,A} + {1'b0,B};
assign CarryOut = tmp[8]; // Carryout flag
always @(*)
begin
    case(ALU_Sel)
        4'b0000: // Addition
            ALU_Result = A + B ;
        4'b0001: // Subtraction
            ALU_Result = A - B ;
        4'b0010: // Multiplication
            ALU_Result = A * B;
        4'b0011: // Division
            ALU_Result = A/B;
        4'b0100: // Logical shift left
            ALU_Result = A<<1;
        4'b0101: // Logical shift right
            ALU_Result = A>>1;
        4'b0110: // Rotate left
            ALU_Result = {A[6:0],A[7]};
        4'b0111: // Rotate right
            ALU_Result = {A[0],A[7:1]};
        4'b1000: // Logical and
    endcase
end

```


INPUT: A-1001(9),B-0011(3)

Alu_SET	Operation	ALU_Result(OUTPUT)
4'b0000: // Addition	A+B	0C
4'b0001: // Subtraction	A-B	06
4'b0010: // Multiplication	A * B	1B
4'b0011: // Division	A/B;	3
4'b0100: // Logical shift left	A<<1;	12(00010010)
4'b0101: // Logical shift right	A>>1	4(00000100)
4'b0110: // Rotate left	{A[6:0],A[7]}	12(00010010)
4'b0111: // Rotate right	{A[0],A[7:1]};	84(10000100)
4'b1000: // Logical and	A & B	01
4'b1001: // Logical or	A B	0B
4'b1010: // Logical xor	A^B	0A
4'b1011: // Logical nor	~(A B)	F4
4'b1100: // Logical nand	~(A & B)	FE
4'b1101: // Logical xnor	~(A ^ B)	F5
4'b1110: // Greater comparison	(A>B)	01
4'b1111: // Equal comparison	(A==B)	00